

1.1.6 Truth Tables

ٹرو تھ ٹیبل (Truth Table) کسی گیٹ یا سرکٹ کے تمام ممکنہ ان پٹ اور ان کے آؤٹ پٹ دکھاتا ہے۔

CS XI

Chapter 1: Computer Systems

Lecture 06 of 20

1.1.6 Truth Tables

LEARN IT

A **truth table** shows **all possible input combinations** and the output for each one, for a logic gate or a circuit. It is the "complete record" of how the circuit behaves.

How to create a truth table:

1. Count the number of inputs (n).
2. Calculate total rows = 2^n .
3. List all input combinations in binary counting order (0, 1, 2, 3 ... in binary).
4. Calculate the output for each combination.

2-input example ($n = 2$, rows = 4)

A	B	Combination
0	0	Row 1
0	1	Row 2
1	0	Row 3
1	1	Row 4

3-input example ($n = 3$, rows = 8)

A	B	C	Decimal
0	0	0	0
0	0	1	1
0	1	0	2
0	1	1	3
1	0	0	4
1	0	1	5
1	1	0	6
1	1	1	7

REMEMBER IT

Quick fill trick for 3 inputs: In column C write 0,1,0,1... (change every row). In column B write 0,0,1,1... (change every 2 rows). In column A write 0,0,0,0,1,1,1,1 (change every 4 rows). For n inputs the leftmost column changes every 2^{n-1} rows.

WORKED EXAMPLE

Make the truth table of a 3-input AND: $Y = A \cdot B \cdot C$.

Step 1: $n = 3$, so rows = $2^3 = 8$.

Step 2: List the 8 combinations in binary order.

Step 3: AND gives 1 only when all inputs are 1, so only row 111 gives 1.

A	B	C	$Y = A \cdot B \cdot C$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

COMMON MISTAKE

Do not list rows in a random order — you may miss or repeat a combination. Always count in binary from 000 to 111. Also remember rows = 2^n , not $2 \times n$: 3 inputs give 8 rows, not 6.

اردو میں سمجھیں

ٹروٹھ ٹیبل (Truth Table) کسی گیٹ یا سرکٹ کے تمام ممکنہ ان پٹ اور ان کے آؤٹ پٹ دکھاتا ہے۔ اگر ان پٹ n ہوں تو قطاریں (Rows) 2 کی طاقت n ہوں گی؛ دو ان پٹ کے لیے 4 اور تین ان پٹ کے لیے 8 قطاریں۔ ان پٹ ہمیشہ بائری ترتیب میں لکھیں۔

CHECK YOURSELF

1. How many rows does a truth table with 4 inputs have?
2. In a 3-input table, what is the 6th row (counting from row 1 = 000)?

Answers: 1. $2^4 = 16$. 2. 101.

Next lecture: 1.1.7 Logic Gates (Basic Gates: AND, OR, NOT)