

1.1.11 Logic Diagrams

لاجک ڈایاگرام دکھاتا ہے کہ گیٹس آپس میں کیسے جڑ کر سرکٹ بناتے ہیں۔

CS XI

Chapter 1: Computer Systems

Lecture 11 of 20

★ Golden

1.1.11 Logic Diagrams ★ Golden

LEARN IT

A **logic diagram** shows how logic gates are connected to create a circuit. It is a "picture" of a Boolean expression. To draw one, use the order of precedence: the operation with the **highest priority is drawn first** (nearest the inputs), and the last operation is the gate that gives the final output.


WORKED EXAMPLE

Example 1: Draw the logic diagram for $Y = A \cdot B + C$.

Step 1: Find the operations: AND ($\cdot$) and OR ($+$).

Step 2: AND has higher precedence than OR, so draw the AND gate first, with inputs A and B. Its output is $A \cdot B$.

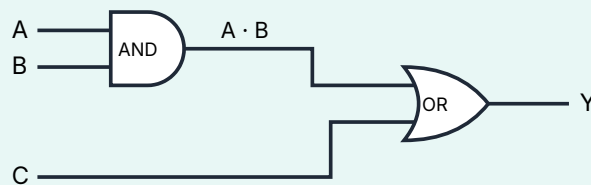Step 3: Draw an OR gate. Feed it $A \cdot B$ and C. Its output is Y.



$Y = A \cdot B + C$: AND first, then OR.


WORKED EXAMPLE

Example 2: Draw the logic diagram for $Y = (A + B) \cdot C'$.

Step 1: Parentheses have the highest priority, so draw the OR gate for $A + B$ first.

Step 2: NOT is next: draw a NOT gate on input C to get C' .

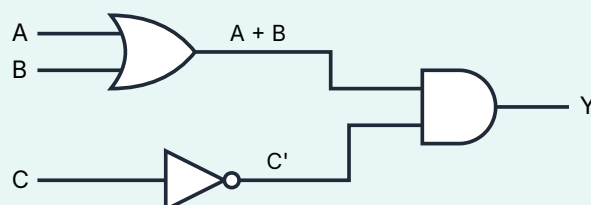Step 3: The last operation is AND: feed $(A + B)$ and C' into an AND gate to get Y.



$Y = (A + B) \cdot C'$: OR and NOT first, then AND.

You can check this circuit against the truth table in 1.1.8 (worked example 2): $Y = 1$ only for rows 010, 100 and 110.

REMEMBER IT

Read the expression and ask "What is done **last**?" That gate goes on the far right, next to Y. Work backwards to the inputs. Count gates: $Y = A \cdot B + C$ needs 2 gates; $Y = (A+B) \cdot C'$ needs 3.

COMMON MISTAKE

Do not draw a separate wire for a variable each time it appears and then leave one unconnected. Every gate input must be joined to an input variable or to another gate's output, and every wire should be clearly labelled in exams.

اردو میں سمجھیں

لاجک ڈایاگرام دکھاتا ہے کہ گیٹس آپس میں کیسے جڑ کر سرکٹ بناتے ہیں۔ ترجیحی ترتیب کے مطابق جو آپریشن پہلے ہوتا ہے اس کا گیٹ پہلے (ان پٹ کے قریب) بنایا جاتا ہے، اور آخری آپریشن کا گیٹ آؤٹ پٹ Y دیتا ہے۔ مثلاً $Y = A \cdot B + C$ میں پہلے AND گیٹ اور پھر OR گیٹ بنتا ہے۔

EXAM TIP

Typical question: "Draw the logic diagram of $Y = \dots$ " and sometimes "also make its truth table" (4–5 marks). Write the precedence steps in one line, draw neat gate symbols with labelled intermediate outputs (like $A \cdot B$), and finish with the truth table. Marks are lost for wrong gate shapes and missing bubbles.

CHECK YOURSELF

1. In $Y = A + B \cdot C$, which gate is drawn first?
2. How many gates are needed for $Y = A' \cdot B$?

Answers: 1. The AND gate (for $B \cdot C$). 2. Two: one NOT gate (for A') and one AND gate.

Next lecture: 1.1.13 Karnaugh Maps (K-Maps)