

1.1.7 Logic Gates (Basic Gates: AND, OR, NOT)

لاچک گیٹس الیکٹرانک سرکٹ ہیں جو بولین آپریشن انجام دیتے ہیں اور تمام ڈیجیٹل نظاموں کی بنیادی اینٹیں ہیں۔

CS XI

Chapter 1: Computer Systems

Lecture 07 of 20

★ Golden

1.1.7 Logic Gates (Basic Gates: AND, OR, NOT) ★ Golden

LEARN IT

Logic gates are electronic circuits that perform Boolean operations. They take one or more input bits and produce one output bit. They are the **building blocks of all digital systems** — a processor contains billions of them.


The three basic gates match the three basic operations: the **AND gate**, the **OR gate** and the **NOT gate** (also called an **inverter**).



$$\text{AND: } Y = A \cdot B$$



$$\text{OR: } Y = A + B$$

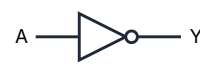

$$\text{NOT: } Y = A'$$

Symbols of the basic gates. AND has a flat back and round front ("D" shape); OR has a curved back and pointed front; NOT is a triangle with a small circle (bubble).

AND gate — $Y = A \cdot B$

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

OR gate — $Y = A + B$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

NOT gate — $Y = A'$

A	Y
0	1
1	0

WORKED EXAMPLE

A school bell circuit. The bell (Y) should ring when the timer says "period over" ($A = 1$) **and** the school is open ($B = 1$).

Step 1: The bell needs both conditions, so use an AND gate: $Y = A \cdot B$.

Step 2: Sunday, timer fires: $A = 1$, $B = 0 \rightarrow Y = 1 \cdot 0 = 0$. No bell.

Step 3: Monday, timer fires: $A = 1$, $B = 1 \rightarrow Y = 1$. The bell rings.

If instead the bell should ring when *either* the timer fires *or* the principal presses a button, you would use an OR gate.

REMEMBER IT

Shortcut: AND output is 0 if *any* input is 0. OR output is 1 if *any* input is 1. Learn just the "special row": AND is 1 only at 11; OR is 0 only at 00.

COMMON MISTAKE

Do not mix up the AND and OR symbols. AND has a **flat** input side (like the letter D). OR has a **curved** input side and a **pointed** output, like a shield or arrowhead.

اردو میں سمجھیں

لاچک گیٹس الیکٹرانک سرکٹ ہیں جو بولین آپریشن انجام دیتے ہیں اور تمام ڈیجیٹل نظاموں کی بنیادی اینٹیں ہیں۔ AND گیٹ صرف تب 1 دیتا ہے جب دونوں ان پٹ 1 ہوں، OR گیٹ صرف تب 0 دیتا ہے جب دونوں ان پٹ 0 ہوں، اور NOT گیٹ ان پٹ کو الٹ دیتا ہے۔

EXAM TIP

You are often asked to "draw the symbol, write the expression and truth table" of a gate (2–3 marks each). Draw neat symbols with labelled inputs A, B and output Y. Write the full truth table in binary order. A frequent MCQ: "Which gate gives 1 only when all inputs are 1?" (AND).

CHECK YOURSELF

1. What is the output of an OR gate when $A = 0$ and $B = 0$?
2. What is another name for the NOT gate?
3. For which input does a 2-input AND gate output 1?

Answers: 1. 0. 2. Inverter. 3. Only $A = 1$, $B = 1$.

Next lecture: 1.1.7 Universal Logic Gates (NAND and NOR)